

Figure 1: A circuit diagram showing a battery connected to two parallel branches. Each branch contains a resistor and a diode in series. The diodes are oriented in opposite directions. The current flows from the positive terminal of the battery, through the top branch, and returns through the bottom branch.

